

**Parul University**  
**Parul Institute of Technology**  
**Department of Mechatronics Engineering**  
**ASSIGNMENT-2**  
**Subject Name: DIGITAL ELECTRONICS**  
**Subject Code: 303105220**  
**(Chapter-2-Boolean Algebra and Mapping Methods)**

1. Given Boolean function  
 $F = x y + x' y' + y' z$ 
  - a. Implement it with only OR & NOT gates
  - b. Implement it with only AND & NOT gates
2. Express following Function in Product of Maxterms  
 $F(x,y,z) = (xy + z)(y + xz)$
3. Explain briefly : SOP & POS, minterm & maxterm, canonical form , (05)  
propagation delay, fan out
4. What is the principle of Duality Theorem?
5. Explain briefly: standard SOP and POS forms.
6. What are Minterms and Maxterms?
7. Define: Noise margin, Propagation delay
8. Reduce the expression:
  - a.  $A+B(AC+(B+C')D)$
  - b.  $(A+(BC)')'(AB'+ABC)$
9. Define : Integrated Circuit and briefly explain SSI, MSI, LSI and VLSI
10. Draw the logic symbol and construct the truth table for each of the .
  - [1] Two input NAND gate
  - [2] Three input OR gate
  - [3] Three input EX-NOR gate
  - [4] NOT gate
11. Give classification of Logic Families and compare CMOS and TTL Families
12. Demonstrate by means of truth tables the validity of the following Theorems of Boolean algebra
  - (i) De Morgan's theorems for three variables
  - (ii) The Distributive law of + over.
13. Express the following functions in sum of min terms and product of max terms:
  - a.  $F(A,B,C,D) = D(A'+B) + B'D$
  - b.  $F(A,B,C) = (A'+B)(B'+C)$
  - c.  $F(x,y,z) = 1$